

$$R_{eq} \text{ for } R_2 + R_3 \text{ in parallel: } \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} = \frac{R_2 R_3}{R_2 + R_3}$$

$$1. \text{ KCL: } I_1 = I_2 + I_3$$

$$\text{KVL: } V - I_1 R_1 - I_2 R_2 = 0$$

$$V - I_1 R_1 - I_3 R_3 = 0$$

$$\text{Solve: } I_1 = \frac{V(R_2 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$


$$I_2 = \frac{V}{R^*} \frac{R_3}{R^*}$$

$$I_3 = \frac{V}{R^*} \frac{R_2}{R^*}$$

$$V_A = V - I_1 R_1$$


Power by source:  $I_1 V$

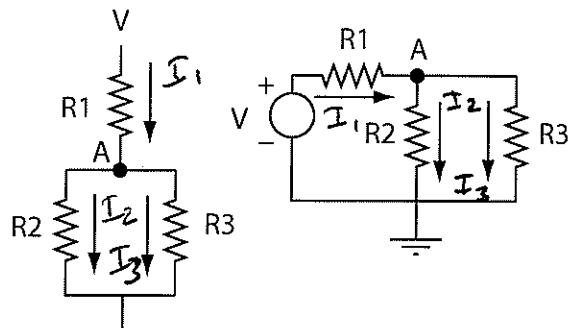Power dissipated by  $R_2$ :  $I_2^2 R_2 = I_2^2 R_2$



2. At  $t=0$ , capacitor acts like a short circuit.  
At  $t=\infty$ , acts like an open circuit.

$$t=0:$$

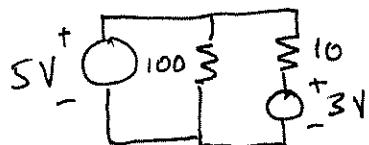

$$\text{KCL: } I_1 + I_2 = I_3$$

$$\text{KVL: } 5 - 100 I_1 = 0 \quad I_1 = 0.05 \text{ A}$$

$$5 - 10 I_2 - 3 = 0 \quad I_2 = 0.2 \text{ A}$$

$$\frac{dV_c}{dt} = \frac{I_1}{C} = 0.5 \frac{\text{V}}{\text{s}}$$

At steady state,  $I_1 = 0$ ,  $V_c = 5V$ .

3V battery charged with power  $3V(I_2) = 0.6W$

5V battery discharged,  $P = 5V(I_2) = 1W$



Energy in capacitor =  $\frac{1}{2} C V_c^2 = 1.25 J$

3.


Voltage test: put leads at B and C

Current test: put leads at C and D

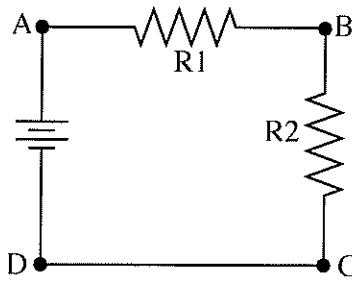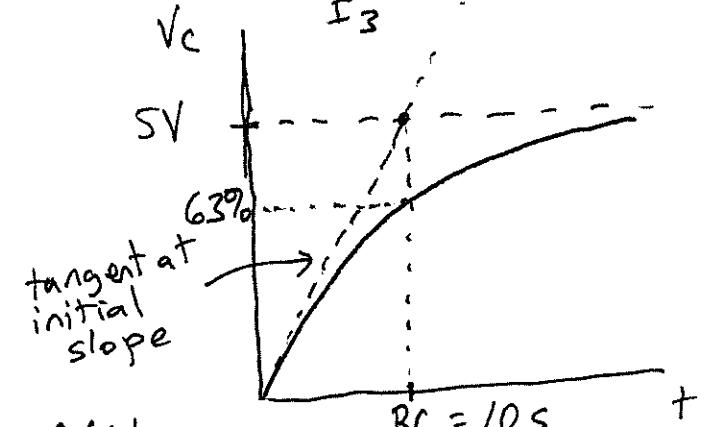and cut the circuit between C and D, so current flows through multimeter.



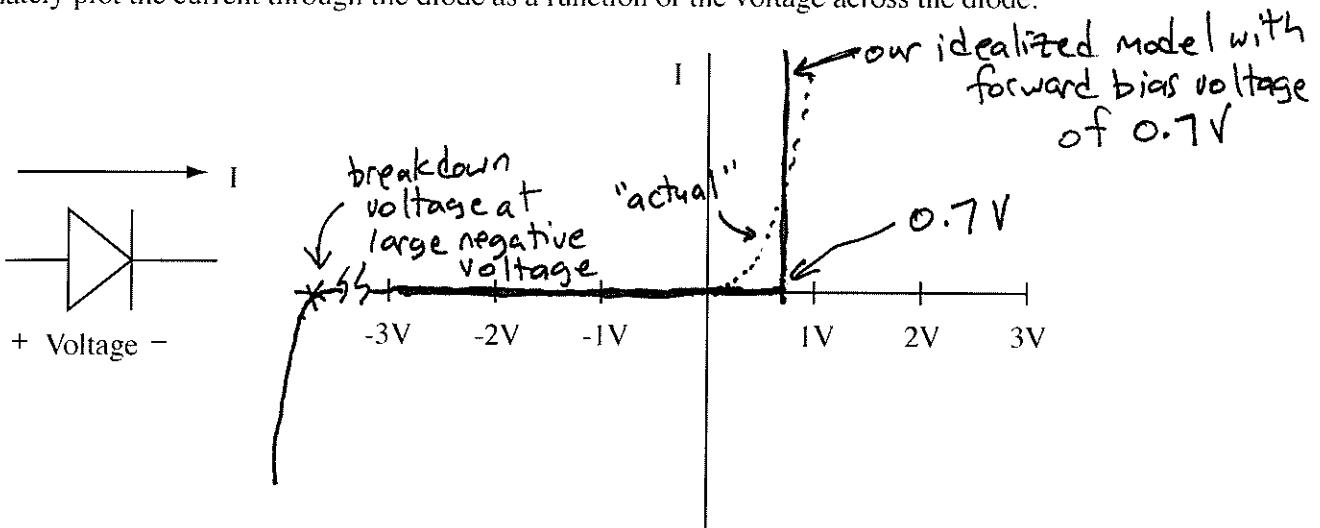4. Approximately plot the current through the diode as a function of the voltage across the diode.



$$5. \text{ KCL: } I = I_1 + I_2$$

$$\text{KVL: } 10 - \frac{dI_1}{dt} - 50I_1 = 0$$

$$10 + V_D = 0$$

$V_D$  is 0.7V if  $I_2 < 0$ , and anything less than 0.7V if  $I_2 = 0$ . ( $I_2$  cannot be  $> 0$ ).

When the switch is closed for a long time, case analysis shows  $I_2 = 0$ . In steady state, inductor is a short circuit, so

$$I_1 = 10 \text{ V} / 50 \Omega = 0.2 \text{ A}. \text{ Inductor energy} = \frac{1}{2} L I^2 = 0.04 \text{ J}.$$

When switch opens,  $I \rightarrow 0$ ,  $I_1$  is unchanged (inductor's current can't change instantly), so

$$I_2 = -I_1 = -0.2 \text{ A}. \text{ Diode is forward biased, so } V_A = 0.7 \text{ V}. \text{ So } V_L = 0.7 \text{ V} - (0.2 \text{ A})(50 \Omega) = -9.3 \text{ V} = L \frac{dI_1}{dt}, \text{ so } \frac{dI_1}{dt} = -4.65 \text{ A/s}$$



6. transistor off:  $V_{in} < V_{BE}$

saturated when  $V_E = V_s - V_{CESsat}$ , or  $V_B = V_s - V_{CESsat} + V_{BE}$ .

So  $I_E = \frac{V_s - V_{CESsat}}{R_2}$ . At transition from linear to saturated,  $I_B = \frac{I_E}{\beta}$ , and  $I_E = I_C + I_B$ .

Solving, get  $I_B = \frac{V_s - V_{CESsat}}{R_2(\beta + 1)}$ , and saturated

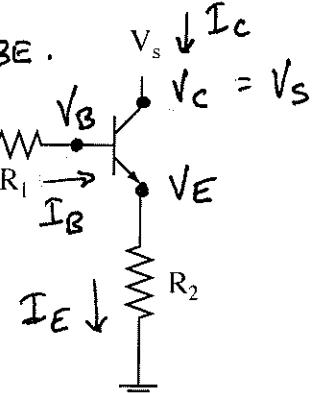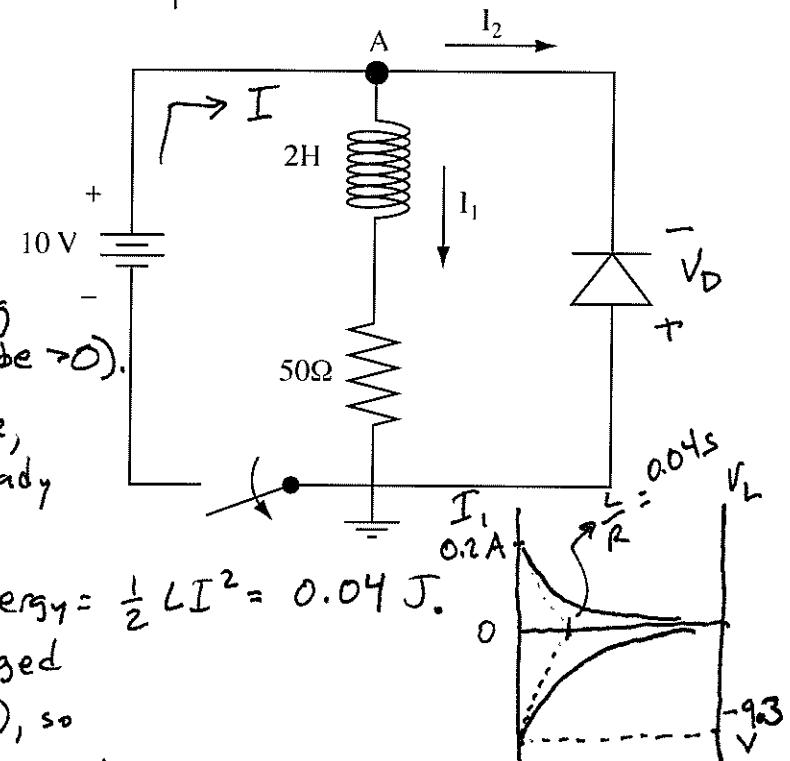if  $V_{in} \geq V_s - V_{CESsat} + V_{BE} + I_B R_1$




$V_B = 0.7V$ . At saturation,  $V_c = 0.2V$ .

7. So  $I_C = \frac{V_s - 0.2V}{R_2} = \beta I_B = \beta \frac{V_{in} - 0.7V}{R_1}$

at transition  
from linear  
to saturated.

$$\beta = \frac{R_1(V_s - 0.2V)}{R_2(V_{in} - 0.7V)}$$

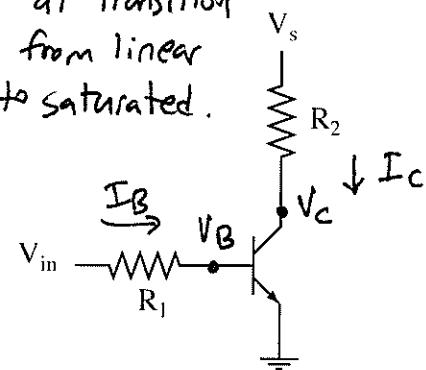$\beta$  must be at least this large for saturation.



8. Steady state, L is a short circuit. ~~so~~ Diode is reverse biased (no current).


$$V_c = V_{CESAT}, I_C = \frac{V - V_{CESAT}}{R_2} = \beta I_B = \beta \left( \frac{V_{in} - V_{BE}}{R_1} \right)$$

Solving for  $V_{in}$ , get  $V_{in} \geq V_{BE} + \frac{(V - V_{CESAT}) R_1}{\beta R_2}$   
for saturation.

When  $V_{in}$  set to zero, transistor turns off, current must flow through diode as shown.

Current through inductor is still  $I_L = (V - V_{CESAT})/R_2$ , but begins to drop.  $V_L - IR_2 - \cancel{V_D} = V_D = 0$ .

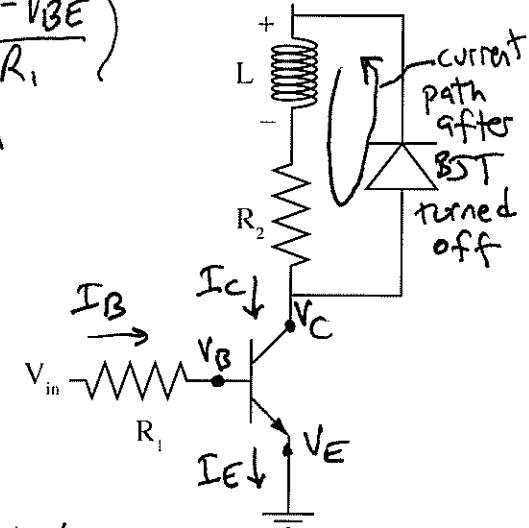Find  $V_L$  from that. Then use  $V_L = L \frac{dI}{dt}$  to find  $\frac{dI}{dt}$ .  
must be negative by the sign convention.



9. Current flows (transistor + LED on) for  $V_{in} > 0.7V$ .


At saturation,  $V_c = (10 - 0.7)V = 9.3V$ ,  $V_E = 9.3 - 0.2 = 9.1V$ ,

$$\text{so } I_E = \frac{9.1V}{100\Omega} = 0.091A = I_C + I_B = 101 I_B.$$

$$I_B = 0.9mA, V_B = 9.1V + 0.7V = 9.8V.$$

$$V_{in} = (I_2 + I_3) 1000\Omega + 9.8V, \text{ so } I_2 = \frac{9.8V}{1000\Omega} = 9.8mA.$$

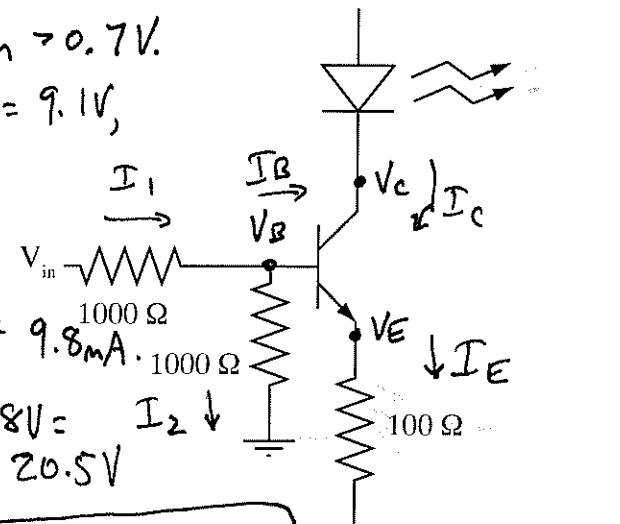
$$\text{Solving, } V_{in} = (10.7mA) 1000\Omega + 9.8V = 20.5V$$



10.  $V_{in}$   $V_{out}$

$$V_{in} \geq 20.5V$$

$$20.5V$$

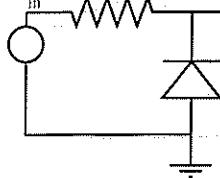

When current flows,  $V_{out} = -0.7V$ .

When current doesn't flow,  
 $V_{out} = V_{in}$ .



11. You can build a simple 3-bit digital-to-analog converter (DAC) using an op-amp as shown at right. The input voltages take values of either 0 or 1 V and represent a 3-bit binary number. At the output you want an analog representation of the 3-bit number,  $V_{out} = -4V_2 - 2V_1 - V_0$ . What resistances  $R_0$ ,  $R_1$ , and  $R_2$  should you use? (Note: real DACs are not made this way.)

Negative feedback, so  $V_A = V_B = 0$ .


No current flows in or out of op-amp inputs, so

$$I_0 + I_1 + I_2 = I_o$$

$$I_0 = V_0 / R_0 \quad V_{out} = V_A - R \left( \frac{V_0}{R_0} + \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$I_1 = V_1 / R_1$$
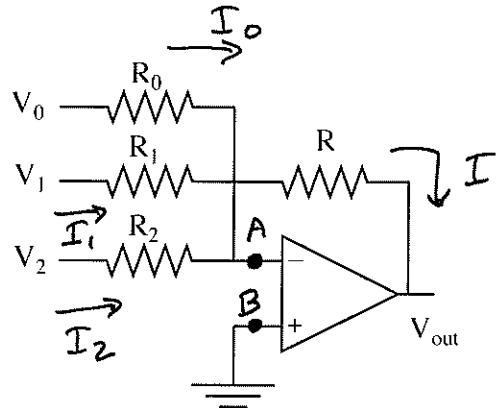
$$I_2 = V_2 / R_2 \quad \text{So choose } R_0 = R, R_1 = \frac{R}{2}, R_2 = \frac{R}{4}$$



12. In the circuit below, give  $V_{out}$  as a function of  $V_1$ ,  $V_2$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $C$  (or some subset of these).

No current in or out of inputs, so  $V_B = I_3 R_3 = 0$ .


Negative feedback, so  $V_A = V_B = 0$ .

No current into - terminal, so  $I_2 = I_1 + I_c$ .

$$V_{out} = V_A - I_2 R_2 = -(I_1 + I_c) R_2$$

$$I_1 = V_1 / R_1$$

$$I_c = C \frac{dV_2}{dt}$$

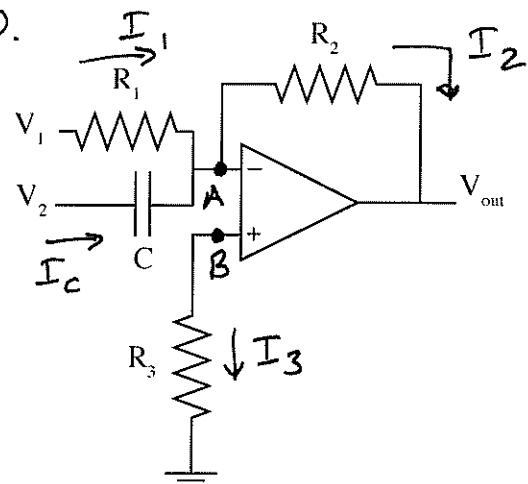

13. In the circuit at right, give  $V_{out}$ .

Negative feedback, so  $V_A = V_B$ .

No current into + input, so  $V_B = V_2$ .

$$I = \frac{V_1 - V_A}{R} = \frac{V_1 - V_2}{R}$$

$$V_{out} = V_A - V_C = V_B - V_C = V_2 - V_C$$

$$V_C = \frac{1}{C} \int I dt = \frac{1}{C} \int \left( \frac{V_1 - V_2}{R} \right) dt$$

